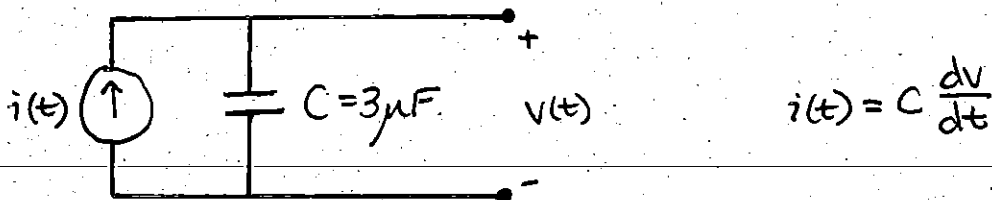


Integrals in Electric Circuits

Application of Integrals in Electric Circuits: (EE 2010)

EXAMPLE: current, voltage, and stored energy in a capacitor



at $t = 0$, $v(0) = 0$ (zero initial voltage)

For $t \geq 0$, $i(t) = 24e^{-40t}$ mA

Find: (a) the voltage $v(t)$

(b) stored energy, $w(t)$, and show $w(t) = \frac{1}{2} C v^2(t)$

Solution:

$$(a) \quad i(t) = C \frac{dv}{dt} \Rightarrow \frac{dv}{dt} = \frac{1}{C} i(t)$$

Integrating both sides,

$$\int_0^t \frac{dv}{dt} dt = \int_0^t \frac{1}{C} i(t) dt$$

$$[v(t)]_0^t = \frac{1}{C} \int_0^t i(t) dt$$

$$v(t) - v(0) = \frac{1}{C} \int_0^t i(t) dt$$

$$v(t) = v(0) + \frac{1}{C} \int_0^t i(t) dt$$

$$\text{Here, } v(0) = 0 \quad C = 3 \times 10^{-6} \text{ F}$$

$$i(t) = 24 e^{-40t} \text{ mA} = 0.024 e^{-40t} \text{ A}$$

$$\Rightarrow v(t) = 0 + \frac{1}{3 \times 10^{-6}} \int_0^t 0.024 e^{-40t} dt$$

$$v(t) = \frac{0.024}{3 \times 10^{-6}} \int_0^t e^{-40t} dt$$

$$v(t) = 8000 \left[-\frac{1}{40} e^{-40t} \right]_0^t$$

$$v(t) = -\frac{8000}{40} (e^{-40t} - 1)$$

$$v(t) = -200(e^{-40t} - 1)$$

$$\therefore v(t) = 200 - 200e^{-40t} \text{ volts}$$

(b) Recall $p(t) = \frac{dW}{dt}$ (energy per unit time)

Integrating both sides,

$$\int_0^t \frac{dW}{dt} dt = \int_0^t p(t) dt$$

$$[W(t)]_0^t = \int_0^t p(t) dt$$

$$W(t) - W(0) = \int_0^t p(t) dt$$

$$W(t) = W(0) + \int_0^t p(t) dt$$

Here, $W(0) = 0$ (no current for $t > 0$)

$$\text{Also, } p(t) = v(t) i(t)$$

$$\therefore p(t) = (200 - 200e^{-40t})(0.024 e^{-40t})$$

$$p(t) = (200 - 200e^{-40t})(0.024e^{-40t})$$

$$p(t) = (200)(0.024e^{-40t}) - (200e^{-40t})(0.024e^{-40t})$$

$$p(t) = 4.8e^{-40t} - 4.8e^{-80t}$$

$$\text{Thus, } w(t) = 0 + \int_0^t (4.8e^{-40t} - 4.8e^{-80t}) dt$$

$$w(t) = 4.8 \left[-\frac{1}{40} e^{-40t} \right]_0^t - 4.8 \left[-\frac{1}{80} e^{-80t} \right]_0^t$$

$$w(t) = -\frac{4.8}{40} (e^{-40t} - 1) - \frac{-4.8}{80} (e^{-80t} - 1)$$

$$w(t) = -0.120e^{-40t} + 0.120 + 0.06e^{-80t} - 0.06$$

$$w(t) = 0.06e^{-80t} - 0.120e^{-40t} + 0.06 \text{ J}$$

$$\text{NOTE: } \frac{1}{2} C V^2(t) = \frac{1}{2} (3 \times 10^{-6}) (200 - 200e^{-40t})^2$$


$$= 1.5 \times 10^{-6} \left((200)^2 - 2(200)(200)e^{-40t} + (200e^{-40t})^2 \right)$$

$$= 1.5 \times 10^{-6} (40000 - 80000e^{-40t} + 40000e^{-80t})$$

$$= 0.06 - 0.120e^{-40t} + 0.06e^{-80t} = w(t)$$

Thus it is proven, $w(t) = \frac{1}{2} C V^2(t)$!

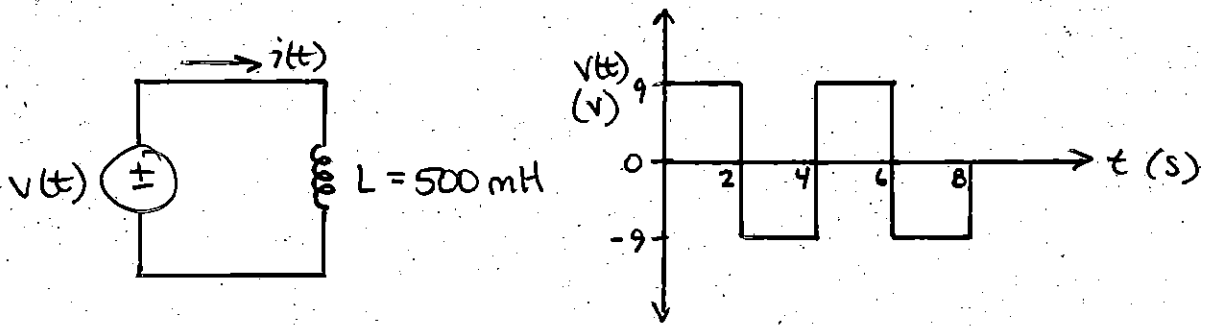EXAMPLE: current and voltage in an inductor.



Knowing $v(t) = L \frac{di}{dt}$, plot the current $i(t)$ using integrals.

Solution: $\frac{di}{dt} = \frac{1}{L} v(t)$

Integrating both sides between 0 and t ,

$$\int_0^t \frac{di}{dt} dt = \frac{1}{L} \int_0^t v(t) dt$$

$$[i(t)]_0^t = \frac{1}{L} \int_0^t v(t) dt$$

$$i(t) - i(0) = \frac{1}{L} \int_0^t v(t) dt$$

also, between any two times t_1 and t_2 ,

$$i_2 - i_1 = \frac{1}{L} \int_{t_1}^{t_2} v(t) dt$$

change in $i(t)$
between t_1 & t_2

area under $v(t)$
from t_1 to t_2

$$0 \leq t \leq 2 \text{ s}: v(t) = 9 \text{ volts} \quad \dots \text{ constant}$$

$$\Rightarrow i(t) = \frac{1}{L} \int v(t) dt \quad \dots \text{ straight line}$$

$$\text{also,} \quad i(2) - i(0) = \frac{1}{L} \int_0^2 v(t) dt$$

$$= \frac{1}{0.50} (2)(9) = 36$$

$$i(2) = i(0) + 36 = 0 + 36 = 36 \text{ A}$$

$$2 \leq t \leq 4 \text{ s}: v(t) = -9 \text{ volts} \quad \dots \text{ constant}$$


$$\Rightarrow i(t) = \frac{1}{L} \int v(t) dt \quad \dots \text{ straight line}$$

$$\text{also,} \quad i(4) - i(2) = \frac{1}{L} \int_2^4 v(t) dt$$

$$= \frac{1}{0.5} (2)(-9) = -36$$

$$i(4) = i(2) - 36 = 36 - 36 = 0$$

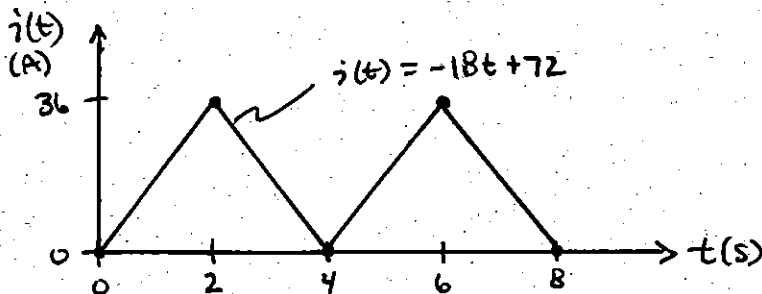Results are identical for $4 \leq t \leq 6 \text{ s}$ and $6 \leq t \leq 8 \text{ s}$




NOTE: The equation of the line in each interval can also be obtained by integration.

$$\text{e.g. } 2 \leq t \leq 4 \text{ s}: \int_2^t \frac{di}{dt} dt = \frac{1}{L} \int_2^t v(t) dt$$

$$[i(t)]_2^t = i(t) - i(2) = \frac{1}{0.5} \int_2^t -9 dt$$

$$i(t) = i(2) + 2[-9t]_2^t$$

$$\Rightarrow i(t) = i(2) + 2(-9t - -9(2)) = 36 - 18t + 36 = \boxed{i(t) = -18t + 72 \text{ A}}$$

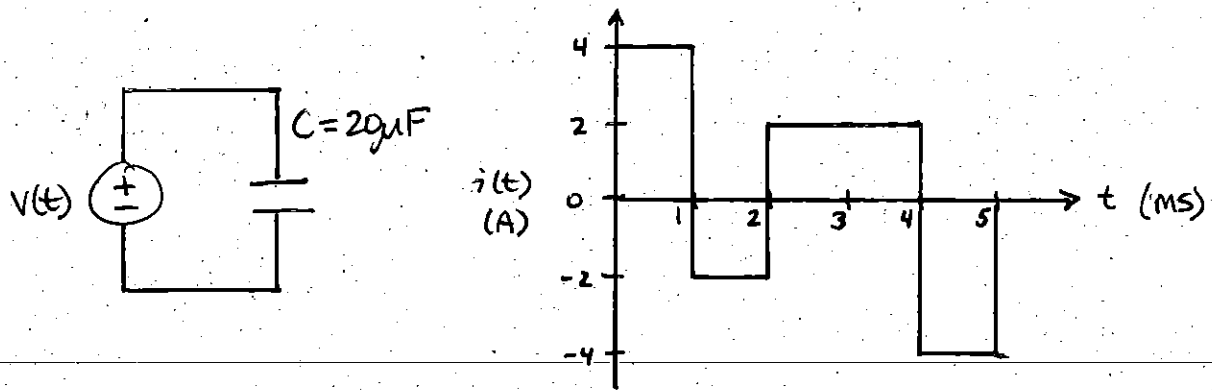EXAMPLE: Current and Voltage in a Capacitor

Sketch voltage $v(t)$, knowing $i(t) = C \frac{dv}{dt}$ or $v(t) = \frac{1}{C} \int i(t) dt$

$0 \leq t \leq 1$ ms: $i(t) = 4$... constant $\therefore v(t) = \frac{1}{C} \int i(t) dt$... straight line

$$\text{also, } v(1) - v(0) = \frac{1}{C} \int_0^1 i(t) dt = \frac{1}{20 \times 10^{-6}} (1 \times 10^{-3})(4) = 200 \text{ V}$$

$$v(1) = v(0) + 200 = 0 + 200 = \underline{200 \text{ volts}}$$

$1 \leq t \leq 2$ ms: $i(t) = -2$... constant $\therefore v(t) = \frac{1}{C} \int i(t) dt$... straight line

$$\text{also, } v(2) - v(1) = \frac{1}{C} \int_1^2 i(t) dt = \frac{1}{20 \times 10^{-6}} (1 \times 10^{-3})(-2) = -100$$

$$v(2) = v(1) + (-100) = 200 - 100 = \underline{100 \text{ volts}}$$

$2 \leq t \leq 4$ ms: $i(t) = 2$... constant $\therefore v(t) = \frac{1}{C} \int i(t) dt$... straight line


$$\text{also, } v(4) - v(2) = \frac{1}{C} \int_2^4 i(t) dt = \frac{1}{20 \times 10^{-6}} (1 \times 10^{-3})(2) = 200$$

$$v(4) = v(2) + 200 = 100 + 200 = \underline{300 \text{ volts}}$$



$4 \leq t \leq 5$ ms: $i(t) = -4$... constant $\therefore v(t) = \frac{1}{C} \int i(t) dt$... straight line

$$\text{also, } v(5) - v(4) = \frac{1}{C} \int_4^5 i(t) dt = \frac{1}{20 \times 10^{-6}} (1 \times 10^{-3})(-4) = -200$$
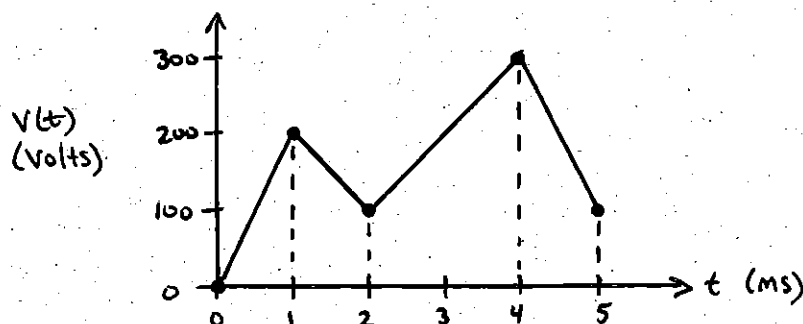
$$v(5) = v(4) - 200 = 300 - 200 = \underline{100 \text{ volts}}$$



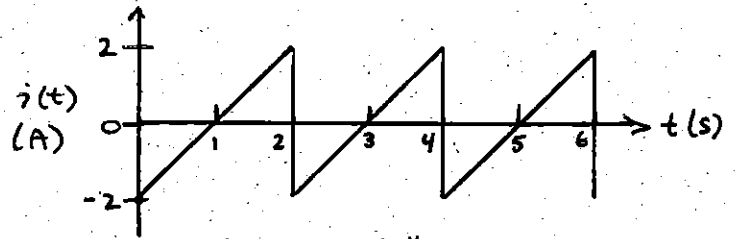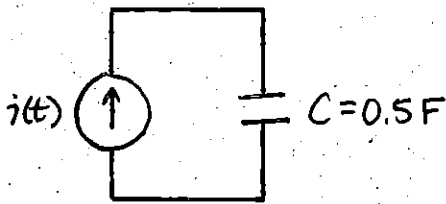EXAMPLE: current and voltage in a capacitor



"Sawtooth" current

Knowing $i(t) = C \frac{dv}{dt}$ ($v(t) = \frac{1}{C} \int i(t) dt$), plot the voltage $v(t)$.
Assume $v_0 = v(0) = 0$

$0 \leq t \leq 1\text{ s}$: $i(t)$... linear $\therefore v(t) = \frac{1}{C} \int i(t) dt$... quadratic

$$\text{also, } v(1) - v(0) = \frac{1}{C} \int_0^1 i(t) dt = \frac{1}{0.5} \left(\frac{1}{2}\right)(1)(-2) = -2$$

$$v(1) = v(0) - 2 = 0 - 2 = -2 \text{ volts}$$

also, since $\frac{dv}{dt} = \frac{1}{C} i(t)$... slope of $v(t)$

$$\left. \begin{array}{l} @t=0, \frac{dv}{dt} = \frac{1}{0.5}(-2) = -4 \\ @t=1, \frac{dv}{dt} = \frac{1}{0.5}(0) = 0 \end{array} \right\} \begin{array}{l} v(t) \text{ is decreasing} \\ \text{w/ slope of zero @ } t=1\text{ s.} \end{array}$$

$1 \leq t \leq 2\text{ s}$: $i(t)$... linear $\therefore v(t) = \frac{1}{C} \int i(t) dt$... quadratic

$$\text{also, } v(2) - v(1) = \frac{1}{C} \int_1^2 i(t) dt = \frac{1}{0.5} \left(\frac{1}{2}\right)(1)(2) = 2$$

$$v(2) = v(1) + 2 = -2 + 2 = 0 \text{ volts}$$

also since $\frac{dv}{dt} = \frac{1}{C} i(t)$... slope of $v(t)$

$$\left. \begin{array}{l} @t=1, \frac{dv}{dt} = \frac{1}{0.5}(0) = 0 \\ @t=2, \frac{dv}{dt} = \frac{1}{0.5}(2) = 4 \end{array} \right\} \begin{array}{l} v(t) \text{ is increasing} \\ \text{w/ zero slope @ } t=1\text{ s.} \end{array}$$

Results are identical for remaining intervals (periodic function!)

