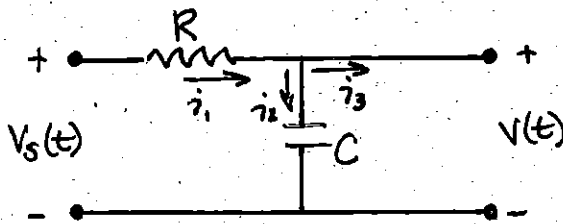


Differential Equations in Electric Systems

EXAMPLE: "Low Pass Filter"



$$i_1 = i_2 + i_3$$

$$i_1 = \frac{V_s(t) - V(t)}{R}$$

$$i_2 = C \frac{dV}{dt} = C \dot{V}(t), \quad i_3 = 0$$

Governing Equation: $RC \dot{V} + V(t) = V_s(t)$... First Order D.E.

given $V_s(t)$, we want to find the output voltage, $V(t)$

also, suppose that $V_s(t) = E \sin \omega t$, $V(0) = 0$

$$RC \dot{V} + V(t) = E \sin \omega t \quad ; \quad V(0) = 0$$

(1) Transient Solution: RHS = 0, $RC \dot{V} + V(t) = 0$

assume, $V_{\text{trans}}(t) = e^{st}$

$$\dot{V}_{\text{trans}}(t) = s e^{st}$$

$$RC s e^{st} + e^{st} = 0 \Rightarrow e^{st} (RCs + 1) = 0$$

$$\therefore s = -\frac{1}{RC}$$

$$\therefore V_{\text{trans}}(t) = C_1 e^{-\frac{1}{RC}t}$$

(dies out as $t \rightarrow \infty$)

(2) Steady-state Solution: since forcing function is sinusoid,

we guess $V_{ss} = A \sin \omega t + B \cos \omega t$ (also a sinusoid)

$$\dot{V}_{ss} = A \omega \cos \omega t - B \omega \sin \omega t$$

plugging back into governing differential equation,

$$RC(A\omega\cos\omega t - B\omega\sin\omega t) + A\sin\omega t + B\cos\omega t = E\sin\omega t$$

Grouping terms,

$$(RC\omega A + B)\cos\omega t + (A - RC\omega B)\sin\omega t = E\sin\omega t$$

Comparing coefficients on $\cos\omega t$ & $\sin\omega t$ on both sides

$$\cos\omega t: RC\omega A + B = 0 \Rightarrow B = -RC\omega A \quad \dots (i)$$

$$\sin\omega t: A - RC\omega B = E \quad \dots (ii)$$

plugging (i) into (ii),

$$A - RC\omega(-RC\omega A) = E$$

$$A(1 + (RC\omega)^2) = E \Rightarrow A = \frac{E}{1 + (RC\omega)^2}$$

$$\text{From (i), } B = -RC\omega \left(\frac{E}{1 + (RC\omega)^2} \right) = \frac{-RC\omega E}{1 + (RC\omega)^2}$$

$$\therefore V_{ss}(t) = \frac{E}{1 + (RC\omega)^2} \sin\omega t + \frac{-RC\omega E}{1 + (RC\omega)^2} \cos\omega t$$

OR


$$V_{ss}(t) = \frac{E}{1 + (RC\omega)^2} (\sin\omega t - RC\omega \cos\omega t)$$

Recall we can further simplify addition of sinusoids if we wish as

$$A\sin\omega t + B\cos\omega t = \sqrt{A^2 + B^2} \sin(\omega t + \phi)$$

where,
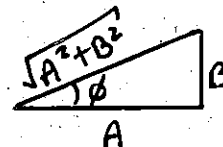
$$\phi = \tan^{-1}\left(\frac{B}{A}\right)$$



$$\Rightarrow \underbrace{\sin \omega t}_{A=1} - \underbrace{RC\omega \cos \omega t}_{B=-RC\omega} = \sqrt{1 + (RC\omega)^2} \sin(\omega t + \phi)$$

$$\text{and } \phi = \arctan 2(-RC\omega, 1) = -\tan^{-1}\left(\frac{RC\omega}{1}\right)$$

$$\Rightarrow V_{ss}(t) = \frac{E}{1 + (RC\omega)^2} \left[\sqrt{1 + (RC\omega)^2} \sin(\omega t + \phi) \right]$$

$$\therefore V_{ss}(t) = \frac{E}{\sqrt{1 + (RC\omega)^2}} \sin(\omega t + \phi), \quad \phi = -\tan^{-1}(RC\omega)$$

(3) Total Solution: $V(t) = V_{trans}(t) + V_{ss}(t)$

$$V(t) = C_1 e^{-\frac{t}{RC}} + \frac{E}{\sqrt{1 + (RC\omega)^2}} \sin(\omega t + \phi), \quad \phi = -\tan^{-1}(RC\omega)$$

(4) Initial Condition: $V(0) = 0$

$$V(0) = C_1 + \frac{E}{\sqrt{1 + (RC\omega)^2}} \sin \phi = 0$$

$$\therefore C_1 = -\frac{E}{\sqrt{1 + (RC\omega)^2}} \sin \phi$$

$$\text{But, } \sin \phi = \frac{B}{\sqrt{A^2 + B^2}} = \frac{-RC\omega}{\sqrt{1 + (RC\omega)^2}}$$

$$\text{So, } C_1 = \frac{-E}{\sqrt{1 + (RC\omega)^2}} \left(\frac{-RC\omega}{\sqrt{1 + (RC\omega)^2}} \right) = \frac{RC\omega E}{1 + (RC\omega)^2}$$

$$\therefore V(t) = \frac{RC\omega E}{1 + (RC\omega)^2} e^{-\frac{t}{RC}} + \frac{E}{\sqrt{1 + (RC\omega)^2}} \sin(\omega t + \phi)$$

$$(\phi = -\tan^{-1}(RC\omega))$$

Why is this circuit called a "low pass" filter?

Steady-state Response:

$$\text{as } t \rightarrow \infty, v(t) \rightarrow v_{ss}(t) = \frac{E}{\sqrt{1 + (RC\omega)^2}} \sin(\omega t + \phi)$$

The input voltage (source) is $v_s(t) = E \sin(\omega t)$

Let us look at the ratio of the output voltage to the input voltage (only their amplitudes):


$$\frac{|v(t)|}{|v_s(t)|} = \frac{E}{\sqrt{1 + (RC\omega)^2}} = \frac{1}{\sqrt{1 + (RC\omega)^2}}$$

$$\text{as } \omega \rightarrow \infty, \frac{|v(t)|}{|v_s(t)|} \rightarrow 0$$

→ this circuit filters out high frequency input!

→ since only low frequencies pass through we call it a "low pass" filter!

EXAMPLE: 2ND order LC circuit

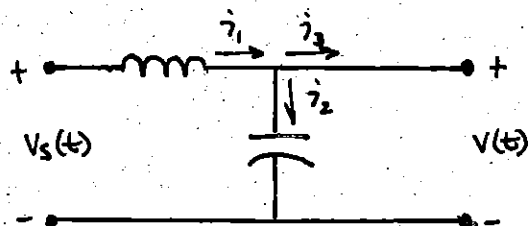

$$i_1 = i_2 + i_3$$

Here, $i_2 = C \frac{dv}{dt}$, $i_3 = 0$

$$\Rightarrow i_1 = C \frac{dv}{dt} + 0 = C \frac{dv}{dt}$$

From KVL,

$$v_s(t) - v_L - v(t) = 0$$

where $v_L = L \frac{di}{dt}$

$$\Rightarrow v_s(t) - L \frac{di}{dt} - v(t) = 0$$

subbing $i_1 = C \frac{dv}{dt}$,

$$v_s(t) - L \frac{d}{dt} \left(C \frac{dv}{dt} \right) - v(t) = 0$$

OR $v_s(t) - LC \frac{d^2v}{dt^2} - v(t) = 0$

Rearranging, $LC \frac{d^2v}{dt^2} + v(t) = v_s(t)$

$$\boxed{LC \ddot{v} + v(t) = v_s(t)}$$

↑
Second order DE.

Suppose $v_s(t) = E \cos \omega t$ and that there is no initial voltage or current across the capacitor

$$\Rightarrow v(0) = 0, \quad i_2 = C \frac{dv(0)}{dt} = 0$$

$$\Rightarrow \dot{v}(0) = 0$$

$$\boxed{LC \ddot{v} + v(t) = E \cos \omega t \quad ; \quad v(0) = 0, \quad \dot{v}(0) = 0}$$

(1) Transient Solution: RHS = 0

$$LC \ddot{v} + v(t) = 0$$

Assume $v_{\text{trans}}(t) = e^{st}$

$$\dot{v}_{\text{trans}}(t) = s e^{st}$$

$$\ddot{v}_{\text{trans}}(t) = s^2 e^{st}$$

$$LC s^2 e^{st} + e^{st} = 0$$

$$e^{st} (LC s^2 + 1) = 0$$

$$s^2 = -\frac{1}{LC} \quad \therefore s = \pm j \sqrt{\frac{1}{LC}}$$

$$\therefore v_{\text{trans}}(t) = C_1 e^{j\sqrt{\frac{1}{LC}}t} + C_2 e^{-j\sqrt{\frac{1}{LC}}t}$$

Via Euler's Formula,

$$\boxed{v_{\text{trans}}(t) = C_3 \cos\left(\sqrt{\frac{1}{LC}}t\right) + C_4 \sin\left(\sqrt{\frac{1}{LC}}t\right)}$$

(2) Steady-state Solution: $LC \ddot{v} + v(t) = E \cos \omega t$

Guess, $v_{\text{ss}}(t) = A \sin \omega t + B \cos \omega t$

$$\ddot{v}_{\text{ss}}(t) = -A \omega^2 \sin \omega t - B \omega^2 \cos \omega t$$

$$LC(-A \omega^2 \sin \omega t - B \omega^2 \cos \omega t) + (A \sin \omega t + B \cos \omega t) = E \cos \omega t$$

Grouping terms,

$$(1 - LC \omega^2) A \sin \omega t + (1 - LC \omega^2) B \cos \omega t = E \cos \omega t$$

$$(1 - LC\omega^2)A \sin \omega t + (1 - LC\omega^2)B \cos \omega t = E \cos \omega t$$

Comparing coefficients on $\sin \omega t$ and $\cos \omega t$ on both sides

$$\sin \omega t: (1 - LC\omega^2)A = 0 \quad \therefore A = 0$$

$$\cos \omega t: (1 - LC\omega^2)B = E \quad \therefore B = \frac{E}{1 - LC\omega^2}$$

$$\therefore V_{ss}(t) = 0 \sin \omega t + \frac{E}{1 - LC\omega^2} \cos \omega t$$

$$\therefore V_{ss}(t) = \frac{E}{1 - LC\omega^2} \cos \omega t$$

(3) Total Solution: $v(t) = v_{trans}(t) + v_{ss}(t)$

$$\therefore v(t) = C_3 \cos\left(\sqrt{\frac{1}{LC}}t\right) + C_4 \sin\left(\sqrt{\frac{1}{LC}}t\right) + \frac{E}{1 - LC\omega^2} \cos \omega t$$

(4) Initial Conditions: $v(0) = 0, \dot{v}(0) = 0$

$$v(0) = C_3 \cos(0) + C_4 \sin(0) + \frac{E}{1 - LC\omega^2} \cos(0)$$

$$C_3 + \frac{E}{1 - LC\omega^2} = 0 \quad \therefore C_3 = -\frac{E}{1 - LC\omega^2}$$

$$\dot{v}(t) = -\sqrt{\frac{1}{LC}} C_3 \sin\left(\sqrt{\frac{1}{LC}}t\right) + \sqrt{\frac{1}{LC}} C_4 \cos\left(\sqrt{\frac{1}{LC}}t\right) - \frac{E\omega}{1 - LC\omega^2} \sin \omega t$$

$$\dot{v}(0) = -\sqrt{\frac{1}{LC}} C_3 \sin(0) + \sqrt{\frac{1}{LC}} C_4 \cos(0) - \frac{E\omega}{1 - LC\omega^2} \sin(0) = 0$$

$$0 + \sqrt{\frac{1}{LC}} C_4 - 0 = 0 \quad \therefore C_4 = 0$$

$$v(t) = -\frac{E}{1 - LC\omega^2} \cos\left(\sqrt{\frac{1}{LC}}t\right) + \frac{E}{1 - LC\omega^2} \cos \omega t$$

$$v(t) = \frac{E}{1 - LC\omega^2} (\cos\omega t - \cos(\sqrt{\frac{E}{LC}} t))$$

NOTE: recall spring-mass problem

$$m\ddot{y} + ky = F\cos\omega t, \quad y(0) = \dot{y}(0) = 0$$

$$\Rightarrow y(t) = \frac{F}{k - m\omega^2} (\cos\omega t - \cos(\sqrt{\frac{k}{m}} t))$$

Here, $LC\ddot{v} + v = E\cos\omega t, \quad v(0) = \dot{v}(0) = 0$

→ Solution is identical with the following corresponding quantities

spring-mass	LC circuit
$y(t)$	$v(t)$
m	LC
k	1
F	E

We have an different physical system, but the math is exactly the same!